

Assignment-3 (ELL201)


Aditya Rahi (2020MT10784)

$$X3 = 8 \% 8 = 0$$

$$X4 = 4 \% 8 = 4$$

Therefore, the sequence to be generated is : {0,0,0,1,0,0}

State Diagram for FSM:

 

Here, **Mealy FSM** is implemented.

Number of flip flops required:

6 states are used to make the FSM. Hence,
No. of flip-flops required $\geq \log_2(\text{no. of states}) = \log_2 6$
 \Rightarrow **No. of flip-flops required = 3**

The values assigned to states are:

A: 000	B: 001
C: 010	D: 011
E: 100	F: 101

State Table:

MSB is Q2, LSB is Q0 and the state in the order is Q2 Q1 Q0.

Current State			Input	Output	Next State			D Flipflops		
Q2	Q1	Q0	X	Y	Q2	Q1	Q0	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	1	0	0	1	0
0	1	0	0	0	0	1	1	0	1	1
0	1	0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1	0	0
0	1	1	1	1	1	0	0	1	0	0
1	0	0	0	0	1	0	1	1	0	1
1	0	0	1	0	1	0	1	1	0	1

1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

The K-Maps are:

D₀ is given by:

$$D_0 = Q_2Q_1'Q_0' + Q_2'Q_1Q_0' + Q_2'Q_0'X$$

Q ₂ Q ₁ \Q ₀ X	00	01	11	10
00	0	1	0	0
01	1	1	0	0
11	0	0	0	0
10	1	1	0	0

D₁ is given by:

$$D_1 = Q_2'Q_1'Q_0 + Q_2'Q_1Q_0'$$

Q ₂ Q ₁ \Q ₀ X	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	0	0	0	0
10	0	0	0	0

D₂ is given by:

$$D2 = Q2'Q1Q0 + Q2Q1'Q0'$$

Q2Q1\Q0X	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	0	0	0
10	1	1	0	0


Y (Output) is given by:

$$Y = Q2'Q1Q0$$

Q2Q1\Q0X	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	0	0	0
10	0	0	0	0

Verilog Code:

Positive Edge triggered D Flip-Flop:

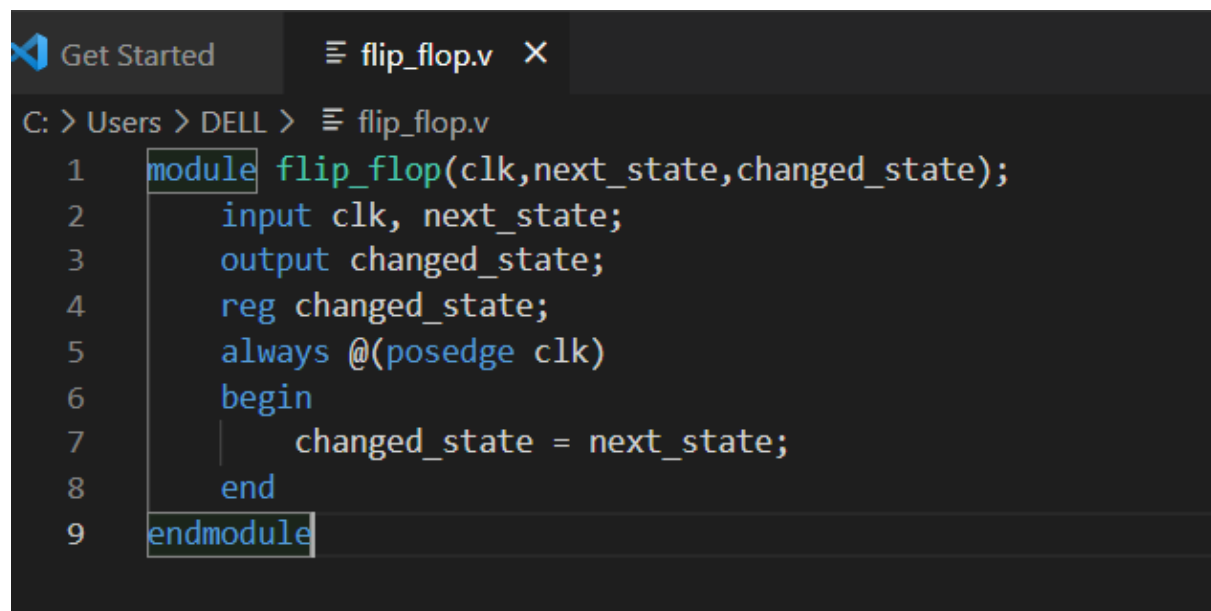

```

Get Started  flip_flop.v X
C: > Users > DELL > flip_flop.v
1  module flip_flop(clk,next_state,changed_state);
2      input clk, next_state;
3      output changed_state;
4      reg changed_state;
5      always @(posedge clk)
6      begin
7          changed_state = next_state;
8      end
9  endmodule

```

Mealy FSM:

```
Get Started  assn3.v  X
C: > Users > DELL > assn3.v
1  module assn3;
2      reg clk;
3      reg xReg;
4      wire [2:0] q;
5      wire yWire;
6      reg Dinput0, Dinput1, Dinput2;
7      assign yWire = (~q[2] & q[1] & q[0]);
8
9      flip_flop FF2(clk,Dinput2,q[2]);
10     flip_flop FF1(clk,Dinput1,q[1]);
11     flip_flop FF0(clk,Dinput0,q[0]);
12
13     always @(negedge clk)
14     begin
15         Dinput2 = (~q[2] & q[1] & q[0])|(q[2] & ~q[1] & ~q[0]);
16         Dinput1 = (~q[2] & ~q[1] & q[0])|(~q[2] & q[1] & ~q[0]);
17         Dinput0 = (q[2] & ~q[1] & ~q[0])|(~q[2] & q[1] & ~q[0])|(~q[2] & ~q[0] & xReg);
18     end
19
20     initial begin
21         $dumpfile("assn3.vcd");
22         $dumpvars(0,assn3);
23         $monitor($time," Input : %b, States : %b %b %b, Output : %b;",xReg,q[2],q[1],q[0],yWire);
24         Dinput0 = 0;
25         Dinput1 = 0;
26         Dinput2 = 0;
27         xReg = 0;
28         clk = 1;
29         #7 xReg = 1;
30         #8 xReg = 0;
31         #8 xReg = 1;
32         #8 xReg = 0;
33         #8 xReg = 1;
34         #8 xReg = 0;
35         #8 xReg = 1;
36         #8 xReg = 0;
37         #8
38         $finish;
39     end
40     always #2 clk = ~clk;
41 endmodule
```

Output:

```
ic_assignment17 opened for output:
 0 Input : 0, States : 0 0 0, Output : 0;
 7 Input : 1, States : 0 0 0, Output : 0;
12 Input : 1, States : 0 0 1, Output : 0;
15 Input : 0, States : 0 0 1, Output : 0;
16 Input : 0, States : 0 1 0, Output : 0;
20 Input : 0, States : 0 1 1, Output : 1;
23 Input : 1, States : 0 1 1, Output : 1;
24 Input : 1, States : 1 0 0, Output : 0;
28 Input : 1, States : 1 0 1, Output : 0;
31 Input : 0, States : 1 0 1, Output : 0;
32 Input : 0, States : 0 0 0, Output : 0;
39 Input : 1, States : 0 0 0, Output : 0;
44 Input : 1, States : 0 0 1, Output : 0;
47 Input : 0, States : 0 0 1, Output : 0;
48 Input : 0, States : 0 1 0, Output : 0;
52 Input : 0, States : 0 1 1, Output : 1;
55 Input : 1, States : 0 1 1, Output : 1;
56 Input : 1, States : 1 0 0, Output : 0;
60 Input : 1, States : 1 0 1, Output : 0;
63 Input : 0, States : 1 0 1, Output : 0;
64 Input : 0, States : 0 0 0, Output : 0;
```

GTK Wave Output:

